




ECUACIONES DIFERENCIALES CON MAPLE



Jhonny Osorio Gallego

CIRCUITO EN SERIE RLC

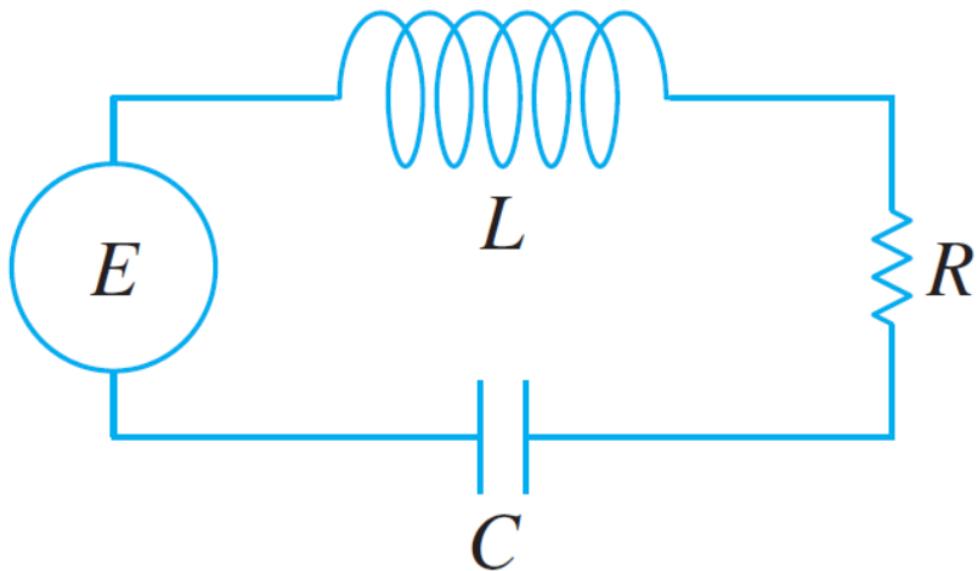

$$Lq'' + Rq' + \frac{1}{C}q = E(t)$$

Ingrese los valores de R, L, C y E

```
> L := 0.5; R := 0; C := 0.005; E := cos(20*x)
      L := 0.5
      R := 0
      C := 0.005
      E := cos(20*x) (1)
```

```
> a := 1; b := convert((R/L), rational); c := convert((1/(C*L)), rational); F := convert((E/L),
      rational);
      a := 1
      b := 0
      c := 400
      F := 2 cos(20*x) (2)
```

>

Ecuación diferencial

> $a \cdot q'' + b \cdot q' + c \cdot q = F$

$$\frac{d^2}{dx^2} q(x) + 400 q(x) = 2 \cos(20x) \quad (3)$$

>

Solución ecuación complementaria

> $a \cdot m^2 + b \cdot m + c = 0$

$$m^2 + 400 = 0 \quad (4)$$

> $\text{solve}(a \cdot m^2 + b \cdot m + c = 0, m)$

$$20i, -20i \quad (5)$$

Conjunto de soluciones ecuación homogénea

> if $b^2 - 4 \cdot a \cdot c \geq 0$ then

$$m1 := \frac{-b + \sqrt{(b)^2 - 4 \cdot a \cdot c}}{2 \cdot a}; m2 := \frac{-b - \sqrt{(b)^2 - 4 \cdot a \cdot c}}{2 \cdot a} \text{ elif } b^2 - 4 \cdot a \cdot c < 0 \\ \text{then } \alpha := \frac{-b}{2 \cdot a}; \beta := \frac{\sqrt{|b^2 - 4 \cdot a \cdot c|}}{2 \cdot a} \\ \text{end if}$$

$$\alpha := 0$$

$$\beta := 20 \quad (6)$$

> if $b^2 - 4 \cdot a \cdot c > 0$ then $q1 := \exp(m1 \cdot x); q2 := \exp(m2 \cdot x)$ elif $b^2 - 4 \cdot a \cdot c = 0$ then $q1 := \exp(m1 \cdot x); q2 := x \cdot \exp(m2 \cdot x)$ elif $b^2 - 4 \cdot a \cdot c < 0$ then $q1 := \exp(\alpha \cdot x) \cdot \cos(\beta \cdot x); q2 := \exp(\alpha \cdot x) \cdot \sin(\beta \cdot x)$ end if

$$q1 := \cos(20x)$$

$$q2 := \sin(20x) \quad (7)$$

Solución complementaria (transitoria)

> $qc := c1 \cdot q1 + c2 \cdot q2$

$$qc := c1 \cos(20x) + c2 \sin(20x) \quad (8)$$

Calculo de wronskianos: w, w1 y w2

> $\text{with(VectorCalculus)} :$

> $W := \text{Wronskian}([q1, q2], x)$

$$W := \begin{bmatrix} \cos(20x) & \sin(20x) \\ -20 \sin(20x) & 20 \cos(20x) \end{bmatrix} \quad (9)$$

> $\text{with(LinearAlgebra)} :$

> $w := \text{combine}(\text{Determinant}(W))$

$$w := 20 \quad (10)$$

$$> WI := \begin{bmatrix} 0 & q2 \\ F & \frac{d}{dx}(q2) \end{bmatrix}$$

$$WI := \begin{bmatrix} 0 & \sin(20x) \\ 2\cos(20x) & 20\cos(20x) \end{bmatrix} \quad (11)$$

$$> w1 := \text{simplify}(\text{Determinant}(WI), \text{trig})$$

$$w1 := -2\sin(20x)\cos(20x) \quad (12)$$

$$> W2 := \begin{bmatrix} q1 & 0 \\ \frac{d}{dx}q1 & F \end{bmatrix}$$

$$W2 := \begin{bmatrix} \cos(20x) & 0 \\ -20\sin(20x) & 2\cos(20x) \end{bmatrix} \quad (13)$$

$$> w2 := \text{combine}(\text{Determinant}(W2), \text{trig})$$

$$w2 := \cos(40x) + 1 \quad (14)$$

Calculo de funciones: u1 y u2

$$> u1 := \text{simplify}\left(\int \frac{w1}{w} dx, \text{trig}\right)$$

$$u1 := \frac{1}{400} \cos(20x)^2 \quad (15)$$

$$> u2 := \text{simplify}\left(\int \frac{w2}{w} dx, \text{trig}\right)$$

$$u2 := \frac{1}{800} \sin(40x) + \frac{1}{20} x \quad (16)$$

>

Solución particular (estado estable)

$$> qp := \text{combine}(u1 \cdot q1 + u2 \cdot q2, \text{trig})$$

$$qp := \frac{1}{400} \cos(20x) + \frac{1}{20} \sin(20x)x \quad (17)$$

Solución general de la ecuación de carga

$$> dsolve(a \cdot q'' + b \cdot q' + c \cdot q = F, \{q(x)\})$$

$$q(x) = \sin(20x)_C2 + \cos(20x)_C1 + \frac{1}{400} \cos(20x) + \frac{1}{20} \sin(20x)x \quad (18)$$

$$> q_ := qc + qp$$

$$q_ := c1 \cos(20x) + c2 \sin(20x) + \frac{1}{400} \cos(20x) + \frac{1}{20} \sin(20x)x \quad (19)$$

Solución general de la ecuación de corriente

$$> i := \frac{d}{dx}(q_)$$

$$i := -20 c1 \sin(20 x) + 20 c2 \cos(20 x) + \cos(20 x) x \quad (20)$$

Condiciones iniciales

> $q0 := 0; i0 := 0$

$$\begin{aligned} q0 &:= 0 \\ i0 &:= 0 \end{aligned} \quad (21)$$

Sistema de ecuaciones

> $\text{simplify}(\text{eval}(q, x=0) = q0)$

$$c1 + \frac{1}{400} = 0 \quad (22)$$

> $\text{simplify}(\text{eval}(i, x=0) = i0)$

$$20 c2 = 0 \quad (23)$$

Solución sistema de ecuaciones

> $\text{solve}(\{\text{eval}(q, x=0) = 0, \text{eval}(i, x=0) = 0\}, \{c1, c2\})$

$$\left\{ c1 = -\frac{1}{400}, c2 = 0 \right\} \quad (24)$$

> $C1 := -\frac{1}{400}; C2 := 0$

$$\begin{aligned} C1 &:= -\frac{1}{400} \\ C2 &:= 0 \end{aligned} \quad (25)$$

Función de carga

> $\text{dsolve}[':-\text{interactive}'](a \cdot q'' + b \cdot q' + c \cdot q = F)$

$$q(x) = \frac{1}{20} \sin(20 x) x \quad (26)$$

> $Q := \text{eval}(q, \{c1 = C1, c2 = C2\})$

$$Q := \frac{1}{20} \sin(20 x) x \quad (27)$$


Función de corriente

> $i := \frac{d}{dx} Q$

$$i := \cos(20 x) x + \frac{1}{20} \sin(20 x) \quad (28)$$


Grafica de la función de carga
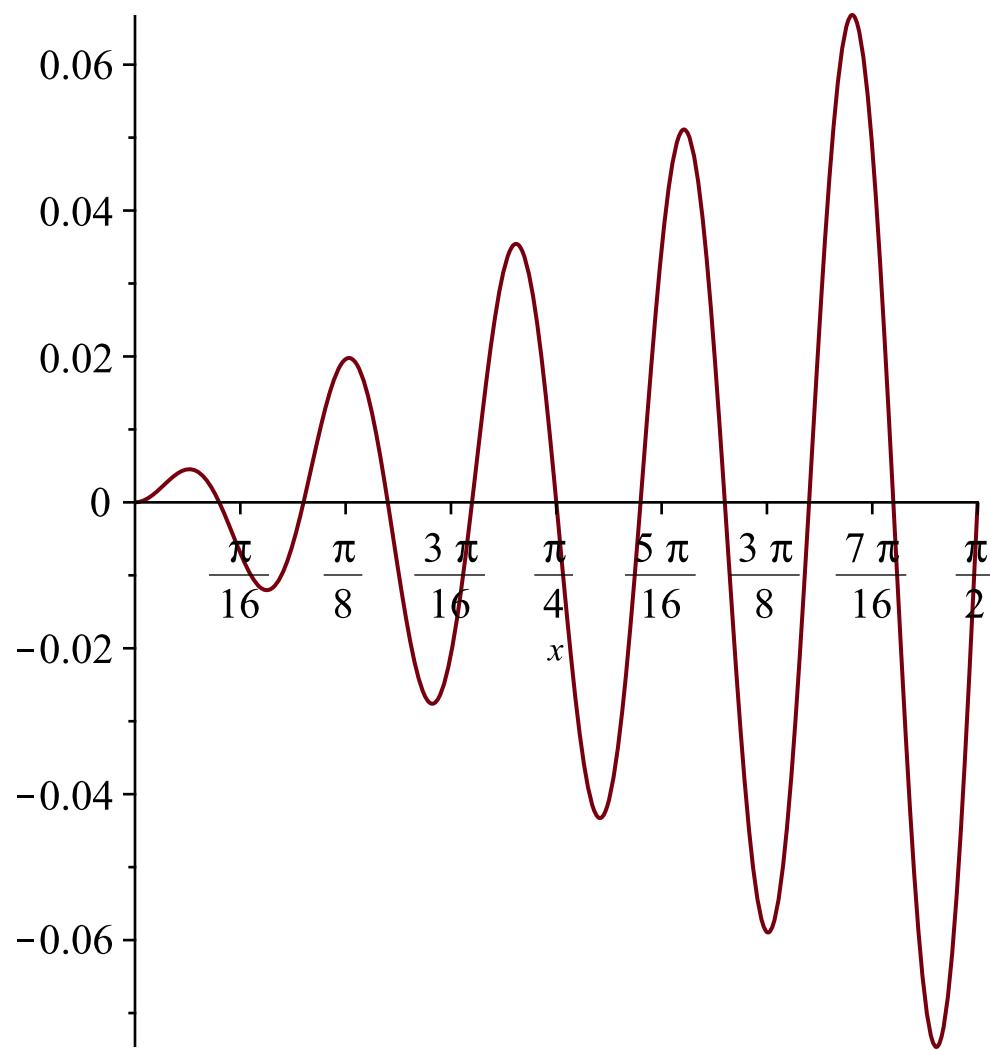
> $\text{plot}\left(\{Q\}, x=0 .. \frac{\pi}{2}\right)$



Grafica de la función de corriente
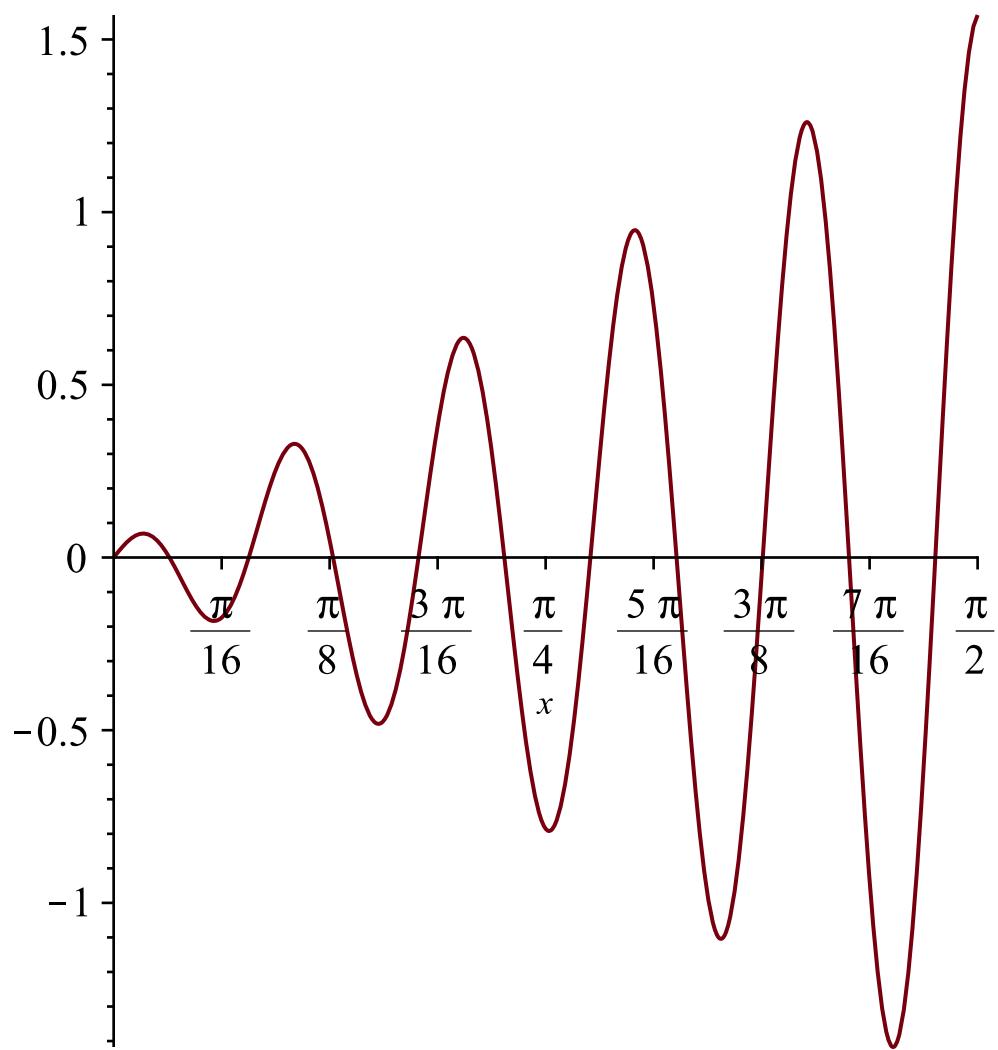
> $\text{plot}\left(\{i_-\}, x=0 .. \frac{\text{Pi}}{2}\right)$



Grafica de la función de carga, solución transitoria y solución particular

> $qc_- := eval(qc, \{c1=C1, c2=C2\})$

$$qc_- := -\frac{1}{400} \cos(20x) \quad (29)$$

> $plot(\{Q, qc_-, qp\}, x=0.. \frac{\text{Pi}}{2})$

